

APPLICATION NOTE

The Influence of Coaxial Inductors on VCO Tuning Bandwidth

Introduction


Ceramic coaxial transmission lines are commonly used to resonate with a varactor in Voltage-Controlled Oscillator (VCO) circuits. When short-circuited at one end and used below the Self Resonant Frequency (SRF), the coaxial line presents an inductive reactance to the VCO. Performance advantages of the coaxial inductor vs discrete wire coils or chip inductors are acknowledged¹. The influence of the coaxial inductor is less obvious on the VCO tuning rate, which is expressed in MHz/Volts.

Unlike an ideal inductor whose reactance varies linearly with frequency, the coaxial inductor reactance increases in a non-linear (tangent-function) manner as the frequency approaches the SRF, as shown in Figure 1.

Although the varactor governs the tuning bandwidth when the inductance is constant, the effective inductance of the coaxial line increases with frequency when approaching the SRF, and opposes the varactor's control. The varactor must be "pushed" further to overcome the increase in effective inductance. For a given control voltage swing, the VCO frequency change is less than with the ideal coil. The tuning bandwidth is reduced when the coaxial inductor is operated near the SRF. Two coaxial lines of a different characteristic impedance (Z_0) but the same SRF have a different effective inductance at f_0 .

Figure 1 shows that for a specified nominal reactance of X_L at the VCO f_0 frequency, a lower coaxial line of Z_0 leads to a lower SRF and a more rapid reactance change in the vicinity of f_0 . This component gives a lower:

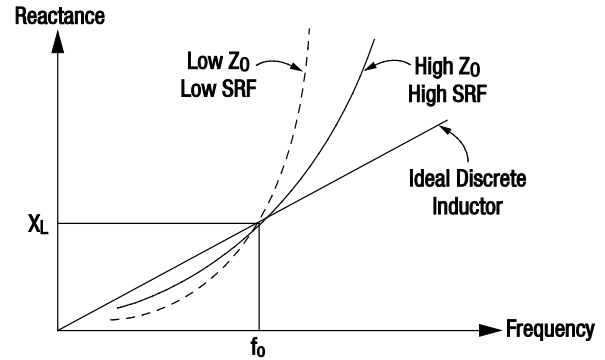- SRF and a more rapid reactance change in the vicinity of f_0 .
- Tuning bandwidth than either a higher-impedance coaxial line or an ideal inductor.



K106

Figure 1. Impedance vs Ideal Inductance

Guidelines

- For widest tuning bandwidth, choose a coaxial inductor with an SRF that is as far as possible above the VCO operating frequency (f_0). Coaxial lines with highest Z_0 and lowest dielectric constant (ϵ_r) have the highest SRF.
- To restrict tuning sensitivity, use a part with the SRF near f_0 . Choose a coaxial inductor with a low Z_0 and high ϵ_r .

¹1.8 GHz Direct Frequency VCO with CAD Assessment, RF Design, p29. Brendan Kelly, February 1993.

APPLICATION NOTE • THE INFLUENCE OF COAXIAL INDUCTORS ON VCO TUNING BANDWIDTH

Copyright © 2013, Trans-Tech Inc., Inc. All Rights Reserved.

Information in this document is provided in connection with Trans-Tech, Inc. ("Trans-Tech"), a wholly-owned subsidiary of Skyworks Solutions, Inc. These materials, including the information contained herein, are provided by Trans-Tech as a service to its customers and may be used for informational purposes only by the customer. Trans-Tech assumes no responsibility for errors or omissions in these materials or the information contained herein. Trans-Tech may change its documentation, products, services, specifications or product descriptions at any time, without notice. Trans-Tech makes no commitment to update the materials or information and shall have no responsibility whatsoever for conflicts, incompatibilities, or other difficulties arising from any future changes.

No license, whether express, implied, by estoppel or otherwise, is granted to any intellectual property rights by this document. Trans-Tech assumes no liability for any materials, products or information provided hereunder, including the sale, distribution, reproduction or use of Trans-Tech products, information or materials, except as may be provided in Trans-Tech Terms and Conditions of Sale.

THE MATERIALS, PRODUCTS, AND INFORMATION ARE PROVIDED "AS IS" WITHOUT WARRANTY OF ANY KIND, WHETHER EXPRESS, IMPLIED, STATUTORY, OR OTHERWISE, INCLUDING FITNESS FOR A PARTICULAR PURPOSE OR USE, MERCHANTABILITY, PERFORMANCE, QUALITY, OR NON-INFRINGEMENT OF ANY INTELLECTUAL PROPERTY RIGHT; ALL SUCH WARRANTIES ARE HEREBY EXPRESSLY DISCLAIMED. TRANS-TECH DOES NOT WARRANT THE ACCURACY OR COMPLETENESS OF THE INFORMATION, TEXT, GRAPHICS, OR OTHER ITEMS CONTAINED WITHIN THESE MATERIALS. TRANS-TECH SHALL NOT BE LIABLE FOR ANY DAMAGES, INCLUDING BUT NOT LIMITED TO ANY SPECIAL, INDIRECT, INCIDENTAL, STATUTORY, OR CONSEQUENTIAL DAMAGES, INCLUDING WITHOUT LIMITATION, LOST REVENUES OR LOST PROFITS THAT MAY RESULT FROM THE USE OF THE MATERIALS OR INFORMATION, WHETHER OR NOT THE RECIPIENT OF MATERIALS HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGE.

Trans-Tech products are not intended for use in medical, lifesaving, or life-sustaining applications, or other equipment in which the failure of the Trans-Tech products could lead to personal injury, death, or physical or environmental damage. Trans-Tech customers using or selling Trans-Tech products for use in such applications do so at their own risk and agree to fully indemnify Trans-Tech for any damages resulting from such improper use or sale.

Customers are responsible for their products and applications using Trans-Tech products, which may deviate from published specifications as a result of design defects, errors, or operation of products outside of published parameters or design specifications. Customers should include design and operating safeguards to minimize these and other risks. Trans-Tech assumes no liability for applications assistance, customer product design, or damage to any equipment resulting from the use of Trans-Tech products outside of stated published specifications or parameters.